

TWO-PORT NETWORK

TKT 419/3


Sem 1 Sidang Akademik 2010/2011

Lecturer: Pn. Wan Nur Suryani Firuz Bt Wan Ariffin (012-4820815)

TWO-PORT NETWORK

- *Terminal equations*
- Two-port parameters
- Relationships among two-port parameters
- Analysis of terminated two-port circuit
- Interconnected two-port circuits

TERMINAL EQUATIONS

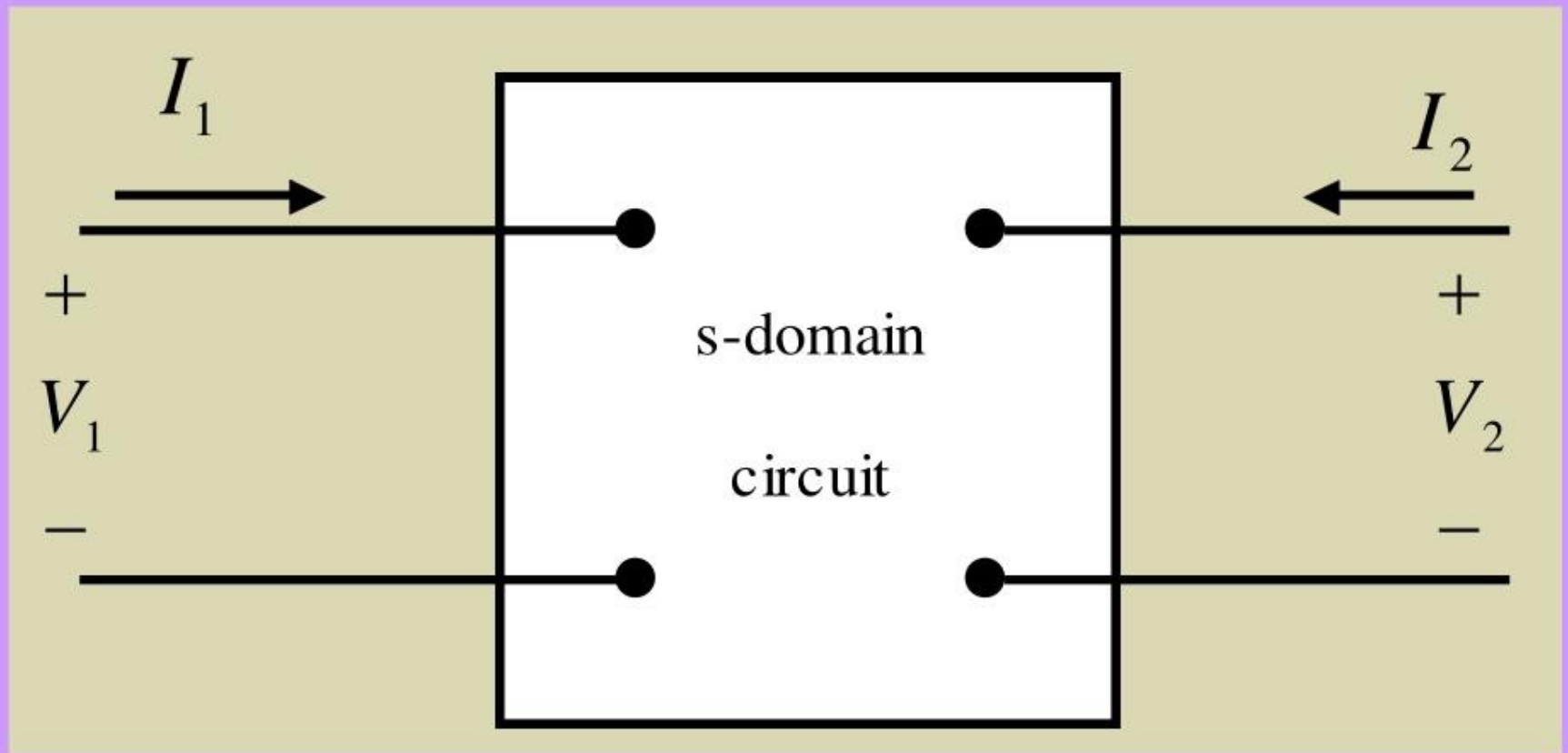

s-domain two-port basic building block

Terminal equations relationships

- **1st Relationship:**

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$



2nd Relationship:

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

3rd Relationship:

$$V_1 = a_{11}V_2 - a_{12}I_2$$

$$I_1 = a_{21}V_2 - a_{22}I_2$$

The top of the slide features a decorative header with six circles arranged in two groups of three. The first group on the left consists of a solid light blue circle, an outlined light blue circle, and another solid light blue circle. The second group on the right consists of a solid light blue circle, an outlined light blue circle, and another solid light blue circle.

4th Relationship:

$$V_2 = b_{11}V_1 - b_{12}I_1$$

$$I_2 = b_{21}V_1 - b_{22}I_1$$



5th Relationship:

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

The top of the slide features two groups of three circles each. The first group on the left consists of a solid light blue circle, an empty white circle with a light blue outline, and another solid light blue circle. The second group on the right consists of a solid light blue circle, an empty white circle with a light blue outline, and a third solid light blue circle.

6th Relationship:

$$I_1 = g_{11}V_1 + g_{12}I_2$$

$$V_2 = g_{21}V_1 + g_{22}I_2$$

TWO PORT NETWORK:

- Terminal equations
- *Two-port parameters*
- Relationships between parameters
- Analysis of terminated two-port circuit
- Interconnected two-port circuits

IMPEDANCE PARAMETERS

• **z parameters**

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \Omega \quad z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \Omega$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \quad \Omega \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} \quad \Omega$$

ADMITTANCE PARAMETERS

y parameters

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad S \quad y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad S$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} \quad S \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} \quad S$$

a parameters

$$a_{11} = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$a_{12} = - \left. \frac{V_1}{I_2} \right|_{V_2=0} \Omega$$

$$a_{21} = \left. \frac{I_1}{V_2} \right|_{I_2=0} S$$

$$a_{22} = - \left. \frac{I_1}{I_2} \right|_{V_2=0}$$

b parameters

$$\begin{array}{ll} b_{11} = \left. \frac{V_2}{V_1} \right|_{I_1=0} & b_{12} = - \left. \frac{V_2}{I_1} \right|_{V_1=0} \quad \Omega \\ b_{21} = \left. \frac{I_2}{V_1} \right|_{I_1=0} \quad S & b_{22} = - \left. \frac{I_2}{I_1} \right|_{V_2=0} \end{array}$$

a and b parameters are called transmission parameters

HYBRID PARAMETERS

h parameters

$$\begin{array}{ll} h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} & \Omega \\ h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} & \\ h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} & \\ h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} & S \end{array}$$


INVERSE HYBRID PARAMETERS

g parameters

$$\begin{array}{ll} g_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0} & S \\ g_{12} = \left. \frac{I_1}{I_2} \right|_{V_1=0} & \\ g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0} & \\ g_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0} & \Omega \end{array}$$

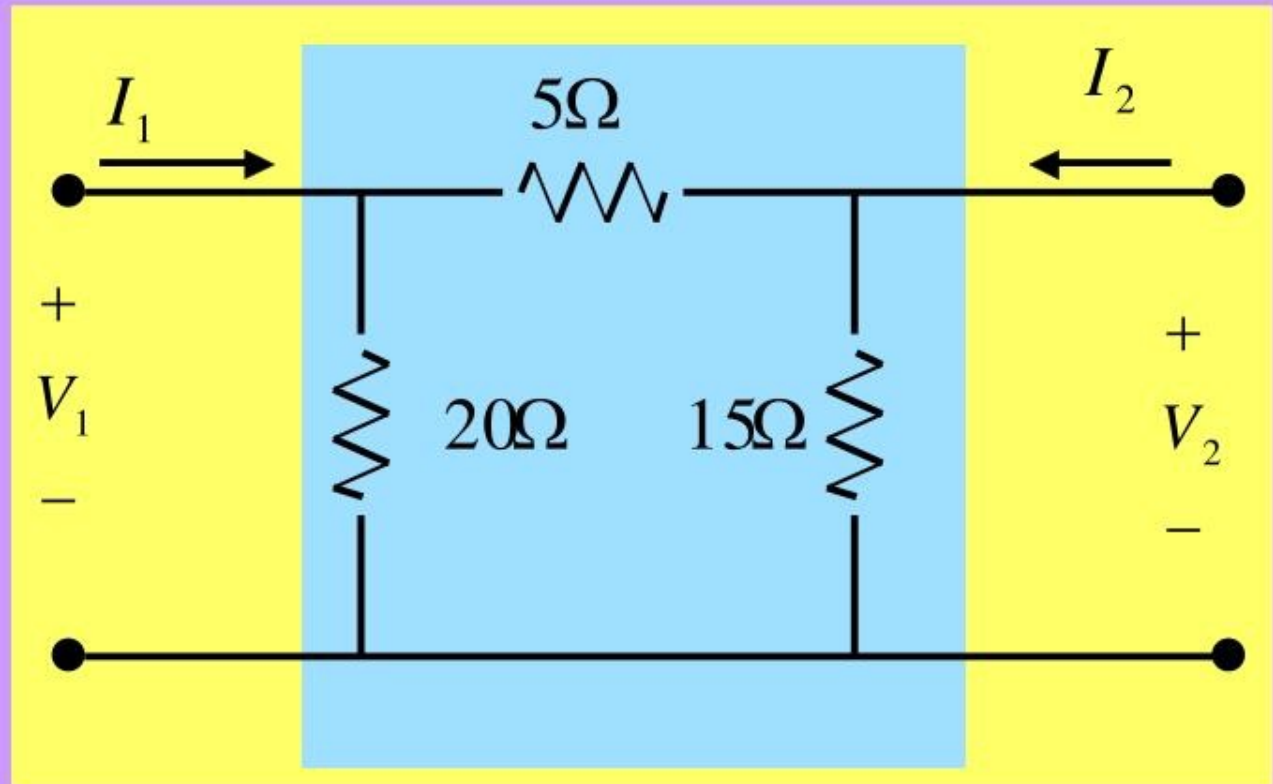Example 1

- Find z parameter for the below circuit:



Solutions:

- When port 2 open-circuit, $I_2=0$
so,

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{20(20)}{40} = 10\Omega$$

When $I_2=0$, thus V_2

$$V_2 = \frac{15}{15+5} V_1 = 0.75V_1$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \frac{0.75V_1}{V_1/10} = 7.5\Omega$$

Now, when $I_1=0$, so

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{15(25)}{40} = 9.375\Omega$$

When port 1 open-circuit, $I_1=0$,
so:

$$V_1 = \frac{20}{5 + 20} V_2 = 0.8V_2$$

$$I_2 = \frac{V_2}{9.375}$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = \frac{0.8V_2}{V_2 / 9.375} = 7.5\Omega$$

TWO-PORT NETWORK

- Terminal equations
- Two-port parameters
- *Relationships between parameters*
- Analysis of terminated two-port circuit
- Interconnected two-port circuits

RELATIONSHIPS BETWEEN PARAMETERS

$$V_1 = \frac{\begin{vmatrix} I_1 & y_{12} \\ I_2 & y_{22} \end{vmatrix}}{\begin{vmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{vmatrix}} = \frac{y_{22}I_1 - y_{12}I_2}{\Delta y}$$



$$V_2 = \frac{\begin{vmatrix} y_{11} & I_1 \\ y_{21} & I_2 \end{vmatrix}}{\begin{vmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{vmatrix}} = \frac{y_{11}I_2}{\Delta y} - \frac{y_{21}I_1}{\Delta y}$$

Compare these two above equations:

$$z_{11} = \frac{y_{22}}{\Delta y} \quad z_{12} = -\frac{y_{12}}{\Delta y}$$

$$z_{21} = -\frac{y_{21}}{\Delta y} \quad z_{22} = \frac{y_{11}}{\Delta y}$$

Find z parameters as functions of a parameters

$$V_2 = \frac{1}{a_{21}} I_1 + \frac{a_{22}}{a_{21}} I_2$$

$$V_1 = \frac{a_{11}}{a_{21}} I_1 + \left(\frac{a_{11}a_{22}}{a_{21}} - a_{12} \right) I_2$$

Therefore,

$$\begin{aligned} z_{11} &= \frac{a_{11}}{a_{21}} & z_{12} &= \frac{\Delta a}{a_{21}} \\ z_{21} &= \frac{1}{a_{21}} & z_{22} &= \frac{a_{22}}{a_{21}} \end{aligned}$$

RECIPROCAL TWO-PORT CIRCUITS

- If a two-port circuit is **reciprocal**, the following relationships exist among port parameters:

$$z_{12} = z_{21} \quad y_{12} = y_{21}$$

$$a_{11}a_{22} - a_{12}a_{21} = \Delta a = 1$$

$$b_{11}b_{22} - b_{12}b_{21} = \Delta b = 1$$

$$h_{12} = -h_{21} \quad g_{12} = -g_{21}$$

Symmetric of a reciprocal two-port circuits

- Following relationships exist among port parameters:

$$z_{11} = z_{22} \quad y_{11} = y_{22}$$


$$a_{11} = a_{22} \quad b_{11} = b_{22}$$

$$h_{11}h_{22} - h_{12}h_{21} = \Delta h = 1$$


$$g_{11}g_{22} - g_{12}g_{21} = \Delta g = 1$$

Example of symmetric two-port circuits


Symmetric tee

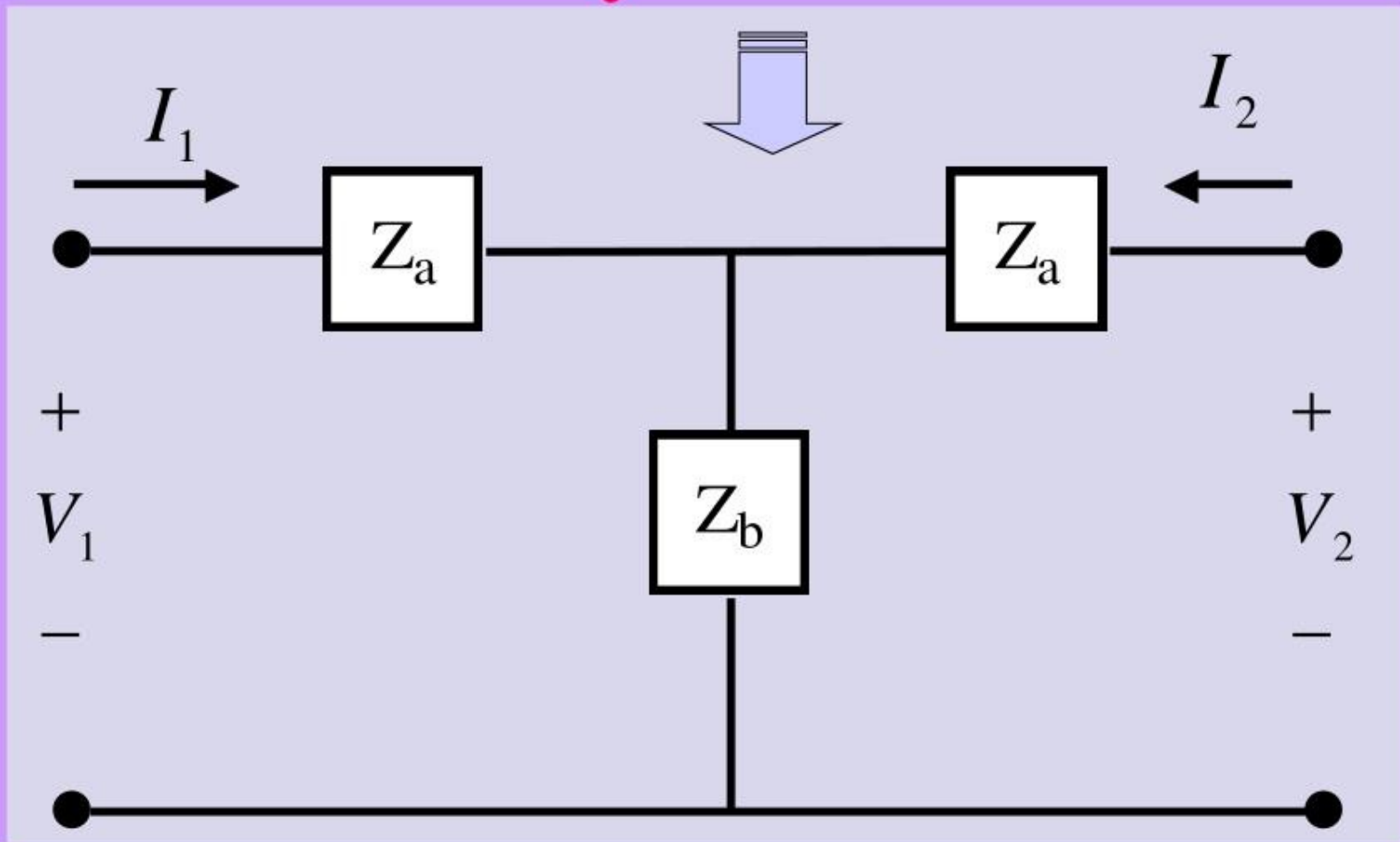


Symmetric pi

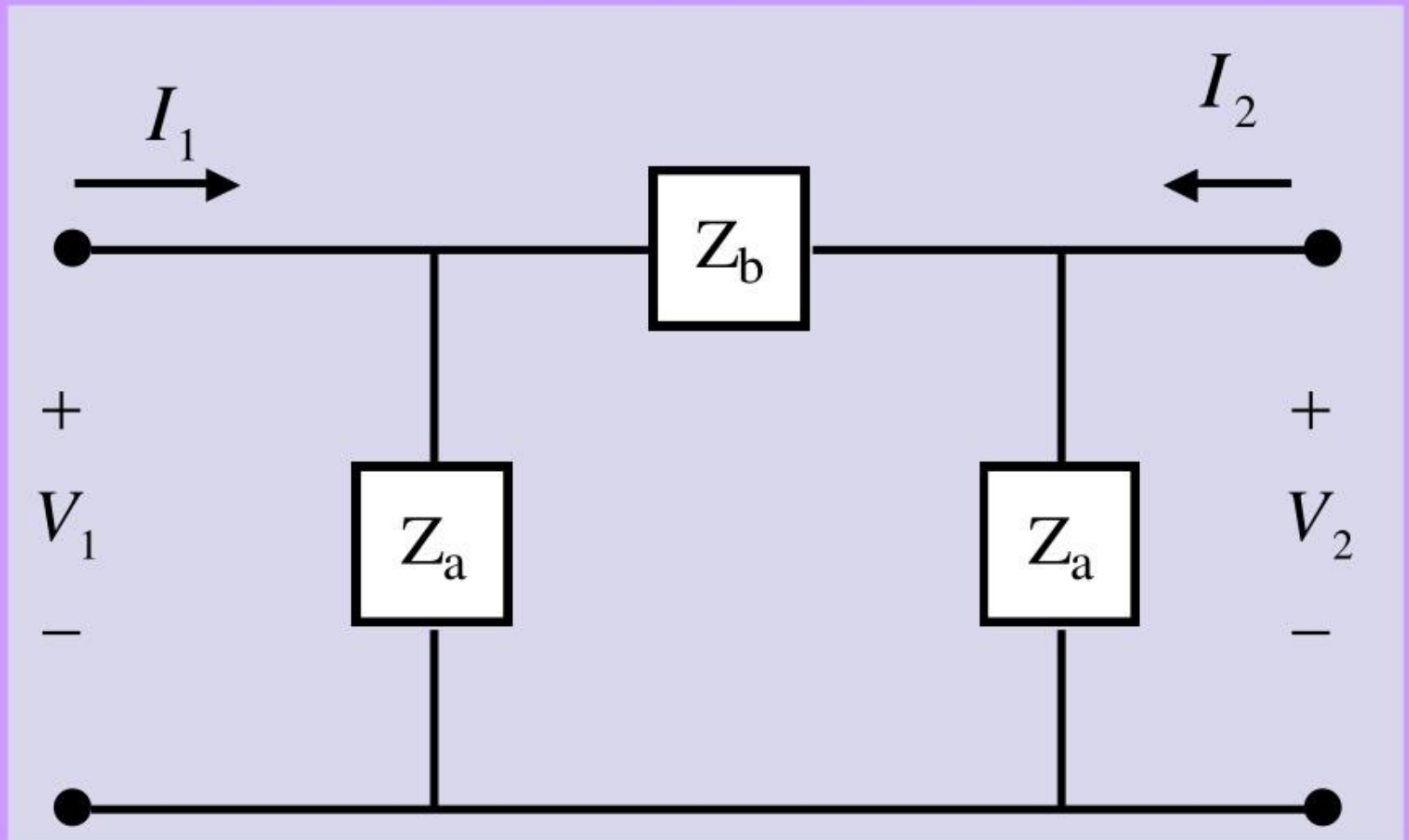

Symmetric bridge tee

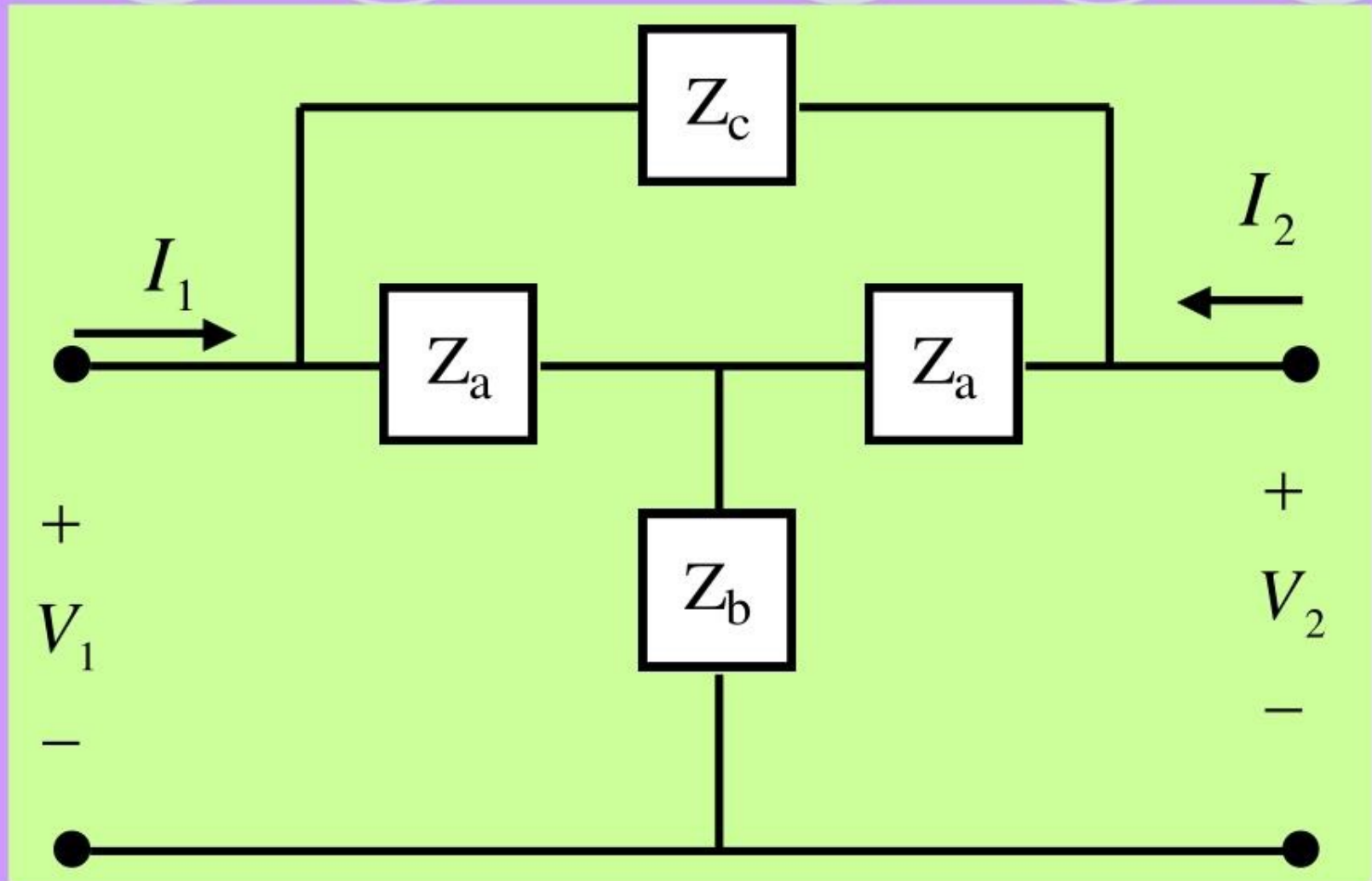


Symmetric lattice

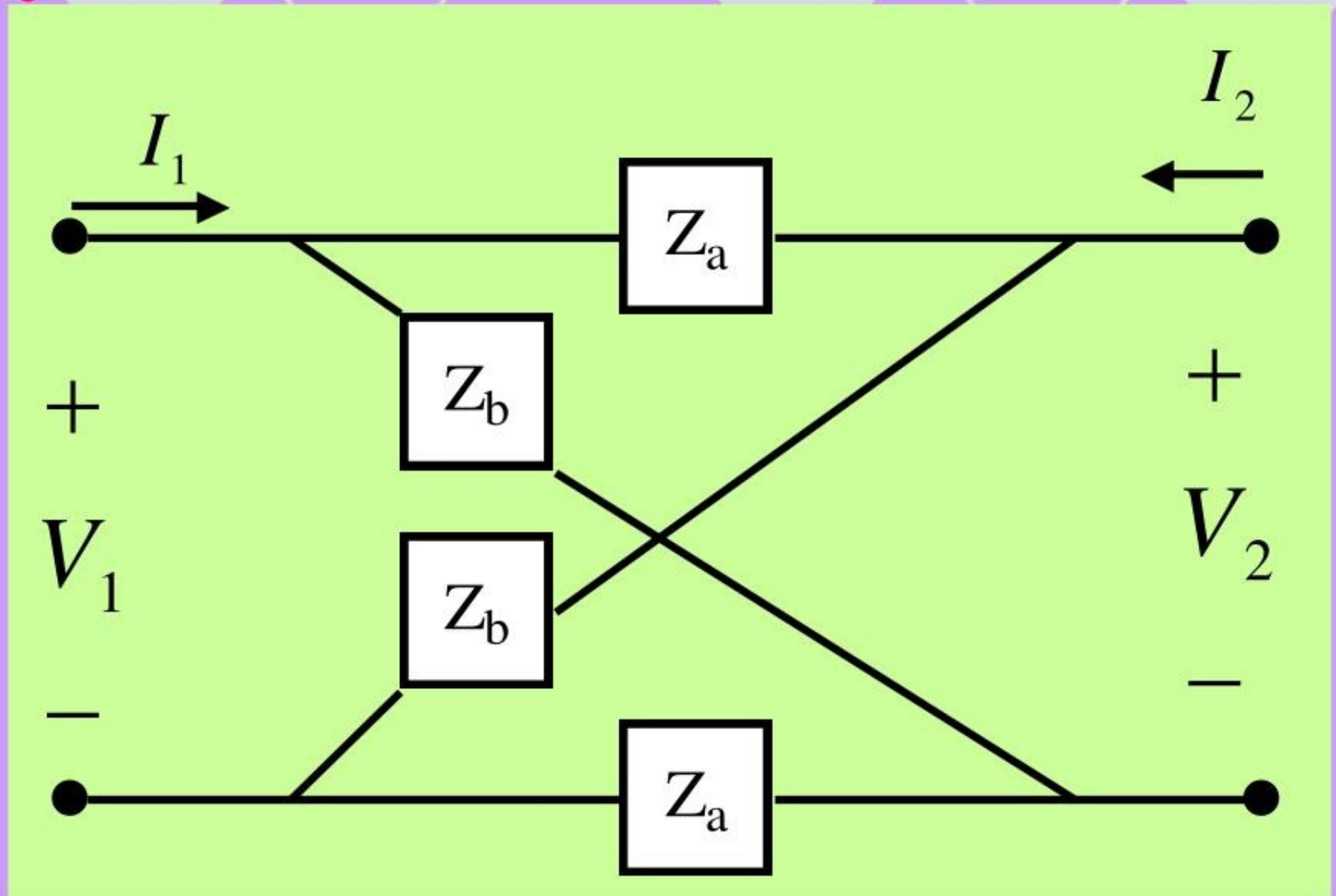

TWO-PORT NETWORK

- Terminal equations
- Two-port parameters
- Relationships between parameters
- **Analysis of terminated two-port circuit**
- Interconnected two-port circuits

ANALYSIS OF TERMINATED TWO-PORT CIRCUITS

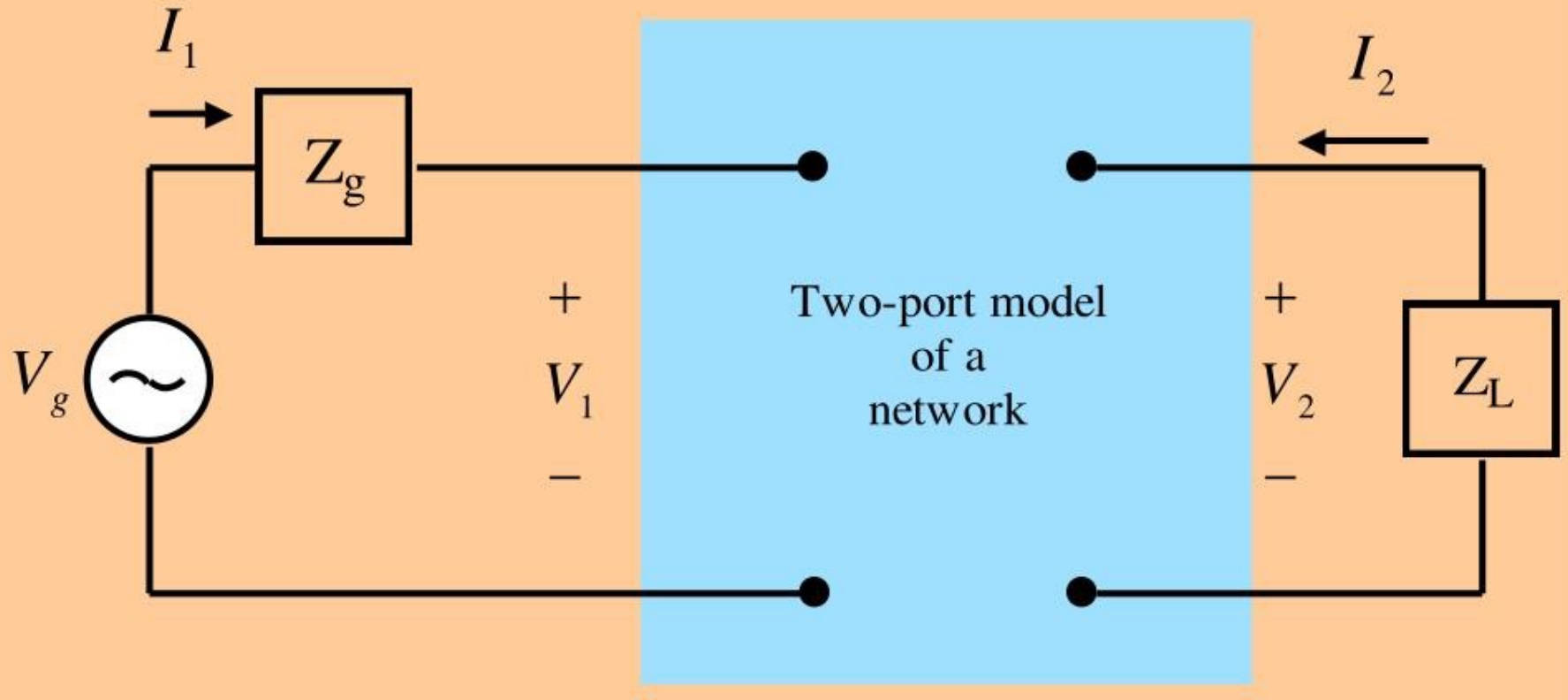

6 characteristics of terminated two-port circuit

- **Input impedance ($Z_{in}=V_1/I_1$) or admittance ($Y_{in}=I_1/V_1$)**
- **Output current, I_2**
- **Thevenin voltage and impedance (Z_{Th} , V_{Th}) with respect to port 2**
- **Current gain I_2/I_1**
- **Voltage gain V_2/V_1**
- **Voltage gain V_2/V_g**

6 characteristics in term of *z parameters*

- 4 parameter equations that describe the circuit:

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

$$V_1 = V_g - I_1 Z_g$$

$$V_2 = -I_2 Z_L$$

1st characteristic (input impedance)

$$I_2 = \frac{-z_{21}I_1}{Z_L + z_{22}}$$

$$Z_{in} = z_{11} - \frac{z_{12}z_{21}}{z_{22} + Z_L}$$

2nd characteristic (output current, I_2)

$$I_1 = \frac{V_g - z_{12}I_2}{z_{11} + Z_g}$$

$$I_2 = \frac{-z_{21}V_g}{(z_{11} + Z_g)(z_{22} + Z_L) - z_{12}z_{21}}$$

3rd characteristic (Thevenin voltage @ impedance)

$$V_2 \big|_{I_2=0} = z_{21} I_1 = z_{21} \frac{V_1}{z_{11}}$$

$$V_2 \big|_{I_2=0} = V_{Th} = V_g \frac{z_{21}}{Z_g + z_{11}}$$

Impedance Thevenin

$$I_1 = \frac{-z_{12}I_2}{z_{11} + Z_g}$$

$$\left. \frac{V_2}{I_2} \right|_{V_g=0} = Z_{Th} = z_{22} - \frac{z_{12}z_{21}}{z_{11} + Z_g}$$

4th characteristic (current gain)

$$\frac{I_2}{I_1} = \frac{-z_{21}}{Z_L + z_{22}}$$

5th characteristic (voltage gain V_2/V_1)

$$V_2 = z_{21}I_1 + z_{22}\left(\frac{-V_2}{Z_L}\right)$$

$$z_{11}I_1 = V_1 - z_{12}\left(\frac{-V_2}{Z_L}\right)$$

$$I_1 = \frac{V_1}{z_{11}} + \frac{z_{12}V_2}{z_{11}Z_L}$$


$$\frac{V_2}{V_1} = \frac{z_{21}Z_L}{z_{11}Z_L + z_{11}z_{22} - z_{12}z_{21}}$$
$$= \frac{z_{21}Z_L}{z_{11}Z_L + \Delta z}$$

6th characteristic (voltage gain V_2/V_g)

$$I_1 = \frac{z_{12}V_2}{Z_L(z_{11} + Z_g)} + \frac{V_g}{z_{11} + Z_g}$$

$$V_2 = \frac{z_{21}z_{12}V_2}{Z_L(z_{11} + Z_g)} + \frac{z_{21}V_g}{z_{11} + Z_g} - \frac{z_{22}}{Z_L}V_2$$




$$\frac{V_2}{V_g} = \frac{z_{21}Z_L}{(z_{11} + Z_g)(z_{22} + Z_L) - z_{12}z_{21}}$$


TWO-PORT NETWORK

- Terminal equations
- Two-port parameters
- Relationships between parameters
- Analysis of terminated two-port circuit
- **Interconnected two-port circuits**

INTERCONNECTED TWO-PORT CIRCUITS

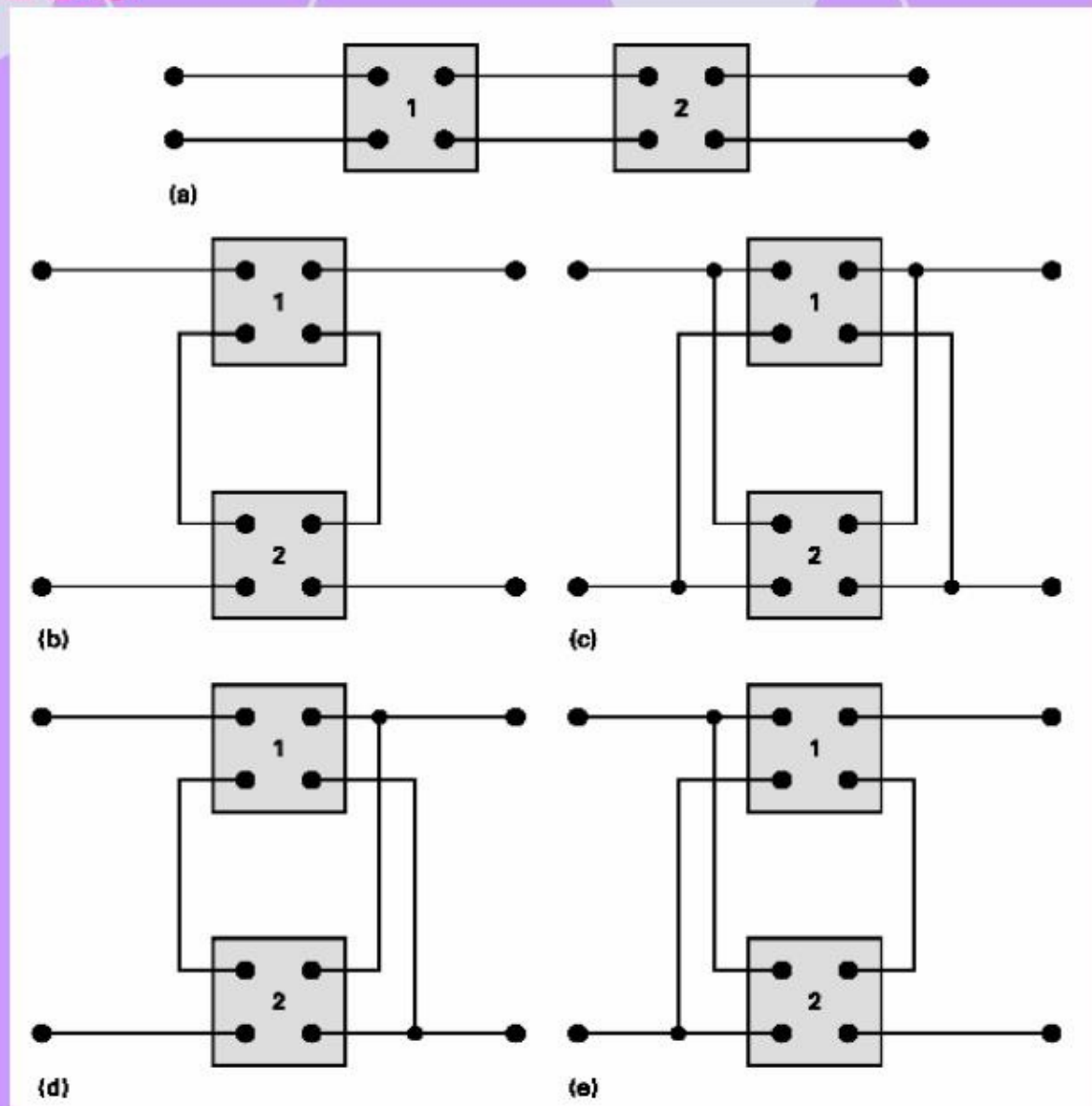

Cascade connection

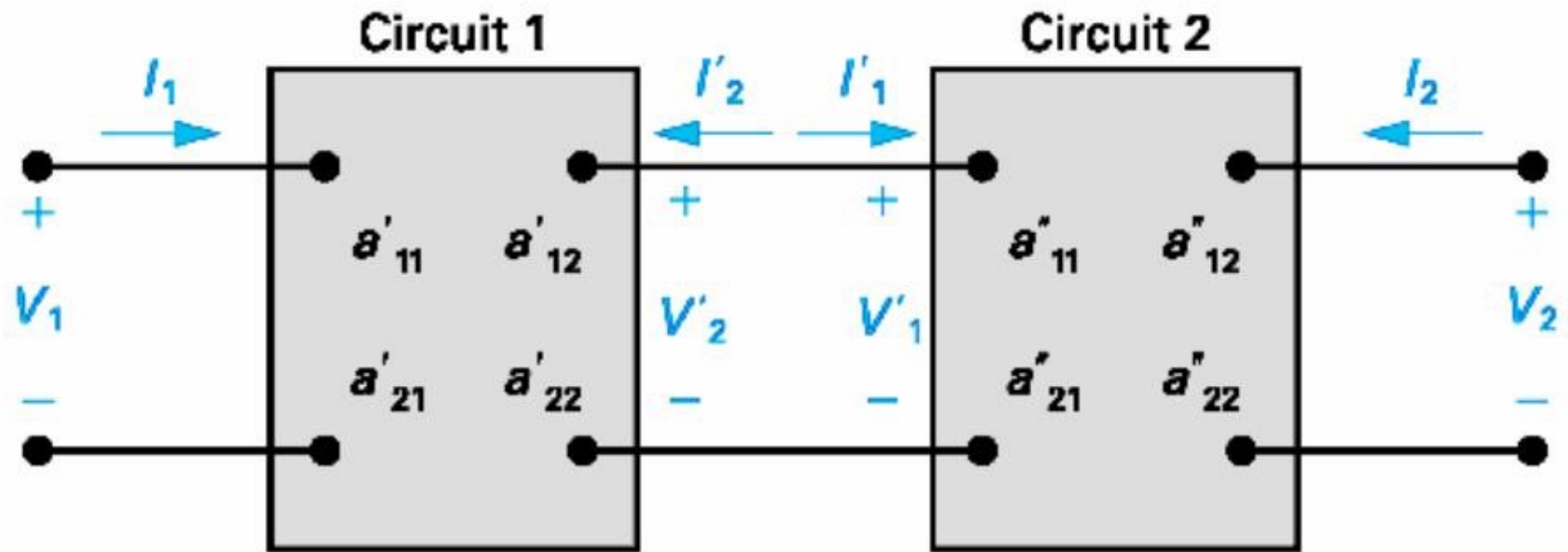

Two-port parameters

$$V_1 = a_{11}V_2 - a_{12}I_2$$

$$I_1 = a_{21}V_2 - a_{22}I_2$$

$$V_1 = a'_{11}V'_2 - a'_{12}I'_2$$

$$I_1 = a'_{21}V'_2 - a'_{22}I'_2$$

Interconnection ($V'_2=V'_1$ and $I'_2=-I'_1$)

$$V_1 = a'_{11}V'_1 + a'_{12}I'_1$$

$$I_1 = a'_{21}V'_1 + a'_{22}I'_1$$

Relationship V'_1 and I'_1 with V_2 and I_2 in second circuit :

$$V'_1 = a''_{11}V_2 - a''_{12}I_2$$

$$I'_1 = a''_{21}V_2 - a''_{22}I_2$$

$$V_1 = (a'_{11}a''_{11} + a'_{12}a''_{21})V_2 - (a'_{11}a''_{12} + a'_{12}a''_{22})I_2$$

$$I_1 = (a'_{21}a''_{11} + a'_{22}a''_{21})V_2 - (a'_{21}a''_{12} + a'_{22}a''_{22})I_2$$

$$a_{11} = a'_{11}a''_{11} + a'_{12}a''_{21}$$

$$a_{12} = a'_{11}a''_{12} + a'_{12}a''_{22}$$

$$a_{21} = a'_{21}a''_{11} + a'_{22}a''_{21}$$

$$a_{22} = a'_{21}a''_{12} + a'_{22}a''_{22}$$

Reference book

- Electric Circuits, James W. Nilsson and Susan A. Riedel, Prentice Hall